



Electrical and Computer Engineering Department  
Network Analysis (ENEE 2311)

**PSPICE Assignment**

Second Semester 2021/2022

30/5/2022

- Solve the two questions in this assignment using PSPICE 9.1 student version.
- **Submit a hardcopy report no later than 15/6/2022;** your report must include a clear snapshot (use snipping tool) of:
  - The circuits schematic in PSPICE with the values of voltages and currents shown at each node and branch for question 1,
  - The circuits schematic in PSPICE with a plot of  $v_o(t)$  for question 2.

Some of the resistors values in the questions are given as (X, Y, and Z); the values of these terms depend on your university ID Number. The last three digits of your university ID number correspond to X, Y, and Z respectively.


Example:

Assume having the following ID number 1110598, then,  $X = 5$ ,  $Y = 9$  and  $Z = 8$ .

In case X or Y or Z corresponds to zero in your ID number, make its value 5 instead of zero.

**Question 1:**


- a) Construct a PSPICE schematic for the circuit shown in Figure 1.
- b) Simulate the schematic and show voltages at each node and current in each branch.

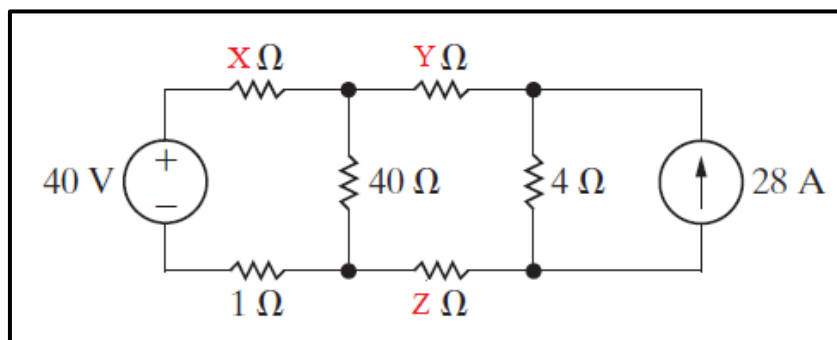

**Figure 1**

**Question 2:**

- Construct a PSPICE schematic for the circuit shown in Figure 2.
- Simulate the schematic and use markers to plot  $V_o(t)$ .

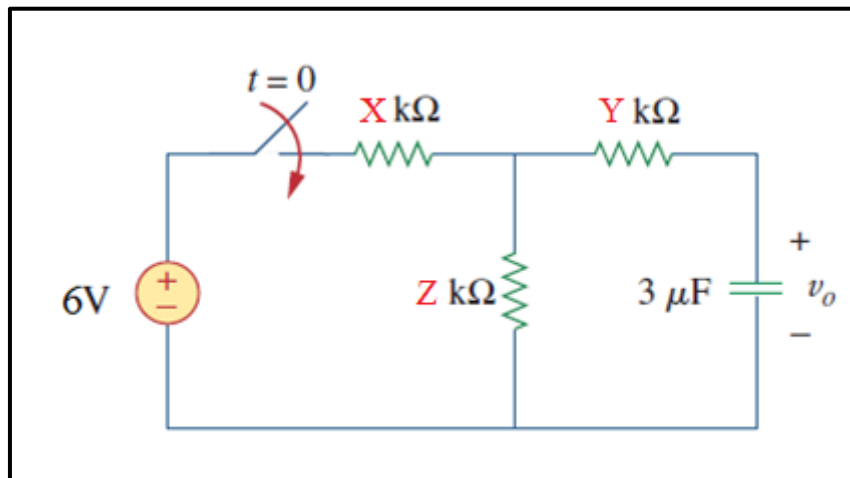

**Figure 2**

**Notes:**

- Assignment solution will vary between students since some parameters depend on the values of X, Y and Z, **any attempt of copying others work will cost you the assignment mark.**
- Although you have enough time, do not start doing your assignment in the last day or last hour!
- If you have questions, do not hesitate to ask your instructor.

Best Wishes 😊